

# Passive High-Pass Filter

Jaeho Cho

*ECE444 - Bioinstrumentation and Sensing*

*The Cooper Union for the Advancement of Science and Art*

New York City, NY

jaeho.cho@cooper.edu

*Abstract—*

*Index Terms—*

## I. INTRODUCTION

## II. METHODOLOGY

From “Table A-1 Element values for low-pass single-resistance-terminated lossless-ladder realizations” in *Introduction to the Theory and Design of Active Filters* [1], the following values are given for a 3rd-order butterworth low-pass filter with a 1 rad/s bandwidth terminated with a resistance of  $R = 1\Omega$ :

$$\begin{aligned}C_1 &= 1.5000 \\L_2 &= 1.3334 \\C_3 &= 0.5000\end{aligned}\tag{1}$$

To transform the low-pass filter into a high-pass filter, the inductors become capacitors with  $C = 1/L$  and the capacitors become inductors with  $L = 1/C$ . The values for the high-pass filter are thus:

$$\begin{aligned}L'_1 &= \frac{1}{C_1} = 0.6667 \\C'_2 &= \frac{1}{L_2} = 0.7500 \\L'_3 &= \frac{1}{C_3} = 2.0000\end{aligned}\tag{2}$$

To denormalize the filter such that the cutoff frequency is  $f_c = 500$  Hz or  $w_c = 2\pi f_c = 3141.59$  rad/s, the component values should be scaled by  $R/w_c$ . Letting  $R = 10K\Omega$  gives the following values:

$$\begin{aligned}L''_1 &= \frac{L'_1}{R * w_c} = 0.2122 \\C''_2 &= \frac{C'_2}{R * w_c} = 0.2387 \\L''_3 &= \frac{L'_3}{R * w_c} = 0.6366\end{aligned}\tag{3}$$

## REFERENCES

- [1] L. P. Huelsman and P. E. Allen, *Introduction to the Theory and Design of Active Filters*. New York: McGraw-Hill, 1980.