

Passive High-Pass Filter

Jaeho Cho

ECE444 - Bioinstrumentation and Sensing

The Cooper Union for the Advancement of Science and Art

New York City, NY

jaeho.cho@cooper.edu

Abstract—

Index Terms—

I. INTRODUCTION

Passive filters are foundational in signal processing, enabling frequency domain control without active elements. High-pass filters (HPFs) allow signals with frequencies higher than a specified cutoff frequency to pass through while attenuating lower frequencies. This study investigates a variant of a passive high-pass filter using two capacitors and one inductor in a novel configuration, assessing its behavior with a standard 1 k Ω load impedance.

II. METHODOLOGY

A. Design Process

From “Table A-1 Element values for low-pass single-resistance-terminated lossless-ladder realizations” in *Introduction to the Theory and Design of Active Filters* [1], the following values are given for a 3rd-order butterworth low-pass filter with a 1 rad/s bandwidth terminated with a resistance of $R = 1\Omega$:

$$\begin{aligned} L_1 &= 1.5000 \\ C_2 &= 1.3334 \\ L_3 &= 0.5000 \end{aligned} \quad (1)$$

To transform the low-pass filter into a high-pass filter, the inductors become capacitors with $C = 1/L$ and the capacitors become inductors with $L = 1/C$. The values for the high-pass filter are thus:

$$\begin{aligned} C'_1 &= \frac{1}{L_1} = 0.6667 \\ L'_2 &= \frac{1}{C_2} = 0.7500 \\ C'_3 &= \frac{1}{L_3} = 2.0000 \end{aligned} \quad (2)$$

To denormalize the filter such that the cutoff frequency is $f_c = 500$ Hz or $\omega_c = 2\pi f_c = 3141.59$ rad/s, the component values should be scaled by R/ω_c . Letting $R = 10k\Omega$ gives the following values:

TABLE I: THEORETICAL COMPONENT VALUES

Component	Ideal	Measured
C_1	100 nF	93.9543 nF
C_2	100 nF	354.231 nF
L_1	0.2122 mH	225.395 mH
R_{ind}	0 Ω	104.016 Ω
R_L	1 k Ω	0.99853 k Ω

$$\begin{aligned} C''_1 &= \frac{C'_1}{R * \omega_c} = 0.2122 \\ L''_2 &= \frac{L'_2}{R * \omega_c} = 0.2387 \\ C''_3 &= \frac{C'_3}{R * \omega_c} = 0.6366 \end{aligned} \quad (3)$$

B. Experimental Setup

68.6271 75.4791
225.395 m

III. RESULTS AND DISCUSSION

A. 4.1 Frequency Response

TABLE II: MEASURED FREQUENCY RESPONSE VALUES

Frequency	V_in	V_out	Linear_Gain	dB_Gain
2	1.05	2.13	2.03	6.14
4	1.05	2.11	2.01	6.06
8	1.05	2.04	1.94	5.77
16	1.05	2.04	1.94	5.77
20	1.05	2.11	2.01	6.06
30	1.05	2.11	2.01	6.06
40	1.05	2.11	2.01	6.06
50	1.05	2.09	1.99	5.98
60	1.05	2.05	1.95	5.81
70	1.05	2.01	1.91	5.64
75	1.05	1.99	1.9	5.55
80	1.05	1.95	1.86	5.38
85	1.05	1.91	1.82	5.2
90	1.05	1.87	1.78	5.01

Frequency	V_in	V_out	Linear_Gain	dB_Gain
95	1.05	1.81	1.72	4.73
100	1.05	1.77	1.69	4.54
105	1.05	1.73	1.65	4.34
110	1.05	1.67	1.59	4.03
115	1.05	1.6	1.52	3.66
120	1.05	1.54	1.47	3.33
125	1.05	1.49	1.42	3.04
130	1.05	1.42	1.35	2.62
135	1.05	1.36	1.3	2.25
140	1.05	1.3	1.24	1.86
145	1.05	1.26	1.2	1.58
150	1.05	1.22	1.16	1.3
160	1.05	1.12	1.07	0.56
170	1.05	1.03	0.98	-0.17
180	1.05	0.95	0.9	-0.87
190	1.05	0.87	0.83	-1.63
200	1.05	0.81	0.77	-2.25
210	1.05	0.75	0.71	-2.92
220	1.05	0.69	0.66	-3.65
230	1.05	0.65	0.62	-4.17
240	1.05	0.61	0.58	-4.72
250	1.05	0.57	0.54	-5.31
270	1.05	0.51	0.49	-6.27
290	1.05	0.47	0.45	-6.98
300	1.05	0.45	0.43	-7.36
350	1.05	0.37	0.35	-9.06
400	1.05	0.3	0.29	-10.88
500	1.01	0.2	0.2	-14.07
600	1.01	0.15	0.15	-16.56
700	1.01	0.13	0.13	-17.81
800	1.01	0.13	0.13	-17.81
900	1.01	0.13	0.13	-17.81
1000	1.01	0.13	0.13	-17.81
1500	1.01	0.13	0.13	-17.81

This paper demonstrates the feasibility and effectiveness of a passive high-pass filter using two capacitors and a single inductor. The filter achieved predictable behavior with a sharp cutoff near the designed frequency and negligible attenuation in the passband. The configuration is suitable for applications requiring compact, passive high-frequency filtration with minimal component count.

IV. DISCUSSION

- The table showed certain values

- To get the proper corner frequency, how did you apply a frequency denormalization?
- To get your inductor value, what impedance denormalization did you apply?
- What component values did that give you?
- What components were you able to find? Did that make you go back and redo the impedance denormalization?

REFERENCES

- [1] L. P. Huelsman and P. E. Allen, *Introduction to the Theory and Design of Active Filters*. New York: McGraw-Hill, 1980.