

Active Low-Pass Filter

Jaeho Cho

ECE444 - Bioinstrumentation and Sensing

The Cooper Union for the Advancement of Science and Art

New York City, NY

jaeho.cho@cooper.edu

Abstract—

Index Terms—Butterworth

I. INTRODUCTION

explain sellen-key topology and butterworth filter

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad (1)$$

$$\frac{1}{Q} = \sqrt{\frac{R_2 C_2}{R_1 C_1}} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} + (1 - K) \sqrt{\frac{R_1 C_1}{R_2 C_2}} \quad (2)$$

$$H_0 = K \quad (3)$$

II. METHODOLOGY

III. RESULTS

Power: 0.02 A x 9 V

plot with measured freq resp and predicted freq resp

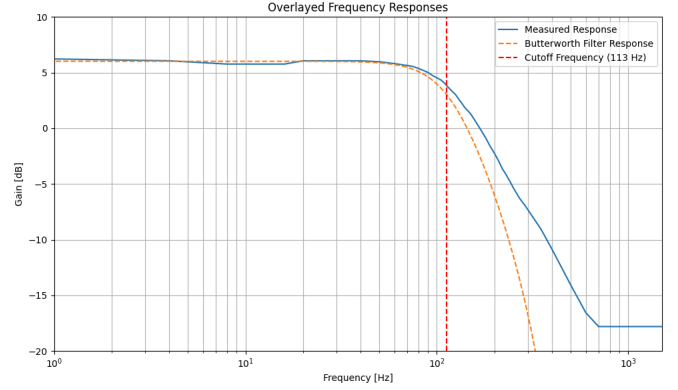


Fig. 2: Measured and Theoretical Frequency Response

TABLE I: FREQUENCY RESPONSE OF THE ACTIVE LOW-PASS FILTER.

IV. DISCUSSION

V. APPENDIX

REFERENCES

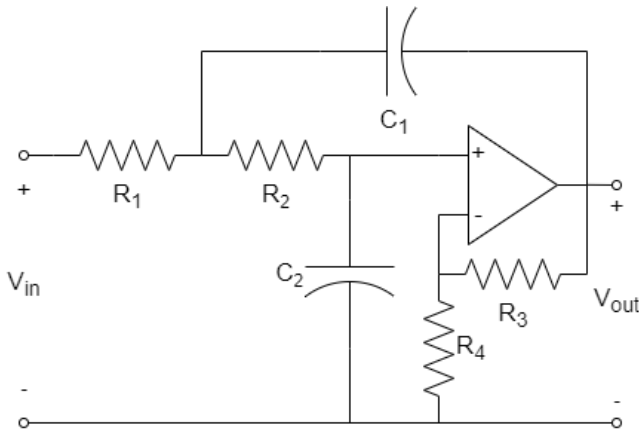


Fig. 1: Sallen-Key topology for the active low-pass filter.